

CmpE 124 Lab 6: Counter Design with D and JK Flip-Flops

Phat Le, 012067666, CmpE 124 Spring 2019, Lab Section 5

Abstract— Using D and JK flip-flop to build a two divide-by-2 circuits, a one-clock-period delay circuit, and a 3 bit ripple down counter circuit.

I. INTRODUCTION

The purpose of this lab is to LogicWorks build two divide-by-2 circuits, a one-clock-period delay circuit, and a 3 bit ripple down counter circuit using 74LS74 and 74LS109.

II. DESIGN METHODOLOGY

S, R, P are just switches and the symbol \nearrow is the next rising edge of the clock that needed to be toggle manually.

A. Parts List

- 74LS163
- 74LS04
- JK Flip-flop 109
- D-type Flip-flop 74

B. Truth Tables

pre	clr	D	clk	q+	qn+
0	0	0	\nearrow	0	1
0	0	0	\nearrow	0	1
0	0	1	\nearrow	1	0
0	0	1	\nearrow	1	0
1	0	-	-	1	
0	1	-	-	0	0

Table 1: D-type Flip-flop

pre	clr	j	k--	clk	q+	qn+
0	0	0	0	\nearrow	q	qn
0	0	0	1	\nearrow	0	1
0	0	1	0	\nearrow	1	0
0	0	1	1	\nearrow	toggle	
1	0	-	-	-	1	0
0	1	-	-	-	0	1

Table 2: JK-type Flip-flop

pre	clr	clk	q+	qn+
0	0	\nearrow	Toggle	
1	0	-	1	0
0	1	-	0	1

pre	clr	P	clk	q+	qn+
0	0	0	\nearrow	q	qn
0	0	1	\nearrow	Toggle	
1	0	-	-	1	0
0	1	-	-	0	1

Table 3: Truth table from lab 7 circuits used to design divided by 2 circuits and 3 bit counter circuit

C. Karnaugh Maps

Karnaugh Maps are not require for this lab.

D. Original and Derived Equations

- $q^+ = s + r'q$

E. Schematics

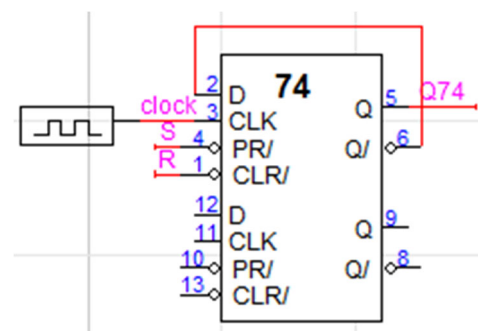


Figure 1: Divide-by-2 circuit using D Flip-Flop

 


Figure 2: Divide-by-2 circuit using JK Flip-Flop

 


Figure 3: One-clock-period delay circuit with D input is Rco from 74LS163

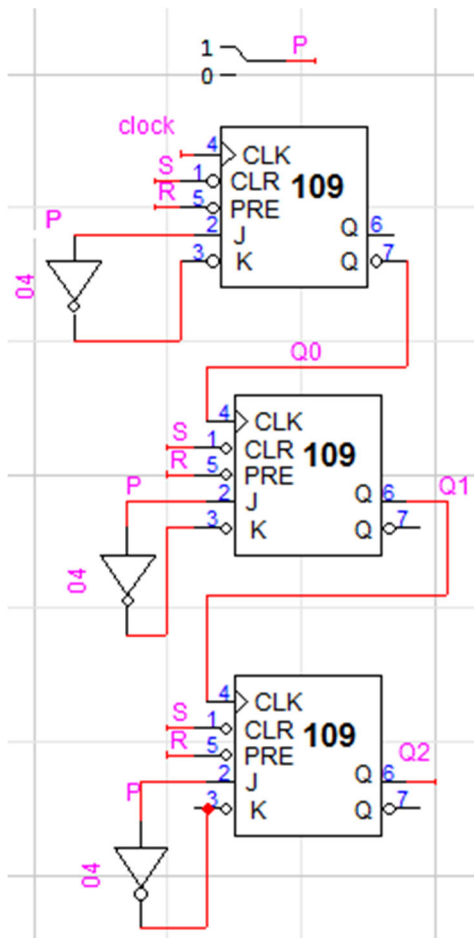


Figure 4: 3-bit ripple down counter circuit

III. TESTING PROCEDURES

1. Apply knowledge from Lab 5 circuit design and Truth Tables. We can see that circuits 7 designed from Lab 6 produces half frequency from the original clock. If we connect the output of a divided by 2 device with the

input of another divided by 2 device, it will produce a counter effect.

2. Use Logic Works to build the circuit.
3. Toggle S, R, P switches to test the output

IV. TESTING RESULTS

 


Figure 5: Waveform signal for divide-by-2 circuit using D Flip-Flop

 


Figure 6: Waveform signal for divide-by-2 circuit using JK Flip-Flop

 


Figure 7: Waveform signal for One-clock-period delay circuit

 


Figure 8: Waveform signal for 3-bit ripple down counter circuit

The testing result as expected for the requirement of lab instruction.

V. CONCLUSION

All circuits were successfully built and produced outputs as expected. To load the data to the 3-bit ripple down counter circuit, PRE and CLR need to be 0 to toggle the output according to table 3.

VI. APPENDICES AND REFERENCES

All the references of Truth table and Schematic are based on Lab 5 and 6 instruction.