

# CMPE 125 Lab Report

## Lab 9 Report

Title System Integration: The Full Calculator

Semester FALL 2019

Date 12-2-19

by

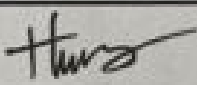



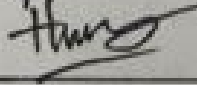



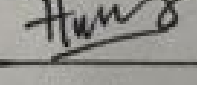



Name HUNG NGUYEN  
(typed)

SID 012392081  
(typed)

Name PHAT LE  
(typed)

SID 012067666  
(typed)

## Lab Checkup Record

Task	Performed By (signature)	Checked By (signature)	Tasks Successfully Completed*	Tasks Partially Completed*	Tasks Failed or Not Performed*
a			100%		
			100%		
b			100%		
			100%		
c			95%		
			100%		

\* Detailed descriptions must be given in the report

## Introduction

The purpose of this lab is to enhance system-level design methodologies, with an emphasis on the control portion, and with the procedure and tools for system-level development. Specifically, the main task is to design, functionally verify, and FPGA hardware validation a calculator system that can perform multiple operations such as addition, subtraction, multiplication, square, increment, decrement and division. However, the report will only cover operations addition, subtraction, multiplication and division due to time constraint.

## Design Methodology

The first task is to design the data path for the FullCalc machine based on the Small\_Calc, integer\_divider, integer\_multiplier designed from previous labs. The data path for this system also include registers to store operands (x,y), output solution(L,H) and the operation selection (f). Furthermore, the system would implement mux to select appropriate outputs coming from different operation modules (Calc, DIV, MUL). Since the maximum is 8-bit when multiplying two 4-bit integer, or division which include the quotient and remainder, the system needs two different 4-bit mux (L, H). Specifically, the datapath would only select the low(L) mux output from the small calculator (Calc) if the operation is addition or subtraction. If it is division, the system would select the low(L) output mux for the quotient, and high(H) output mux for the remainder. For the multiplication, the low(L) mux will select the lower 4-bit of the MUL output (P[3:0]), and the high(H) mux will select the higher 4-bit of the MUL output(P[7:4]).

*Table 1: List of modules for Task 1*

Module	Function
<b>FullCalc_dp</b>	This is the top-level module of the data-path which connects all modules below.
<b>flopenr</b>	This module serves as a register that stores the value for the integer input (X,Y), the operation selection (F), and the final output solution (H,L)
<b>mux4</b>	This module is used to select the proper output of the final result(L)
<b>mux2</b>	This module is used to select the proper output of the final result(H).
<b>Calc</b>	This module performs the subtraction and addition taken from the previous Lab 7.
<b>DIV</b>	This module performs the division operation taken from the previous Lab 8.
<b>MUL</b>	This module performs the multiplication operation taken from the previous Lab 5.
<b>Top_CU</b>	This module is the control unit for the FullCalc machine which control the selection inputs of the

	data path(Go_DIV, Go_Cal, Sel_X, Sel_Y, Sel_F, Sel_H, Sel_L) based on the signal input(Done_calc, Done_DIV, Err, and qF).
<b>FullCalc_tb</b>	This is the testbench module which tests all possible corner cases which goes through all states.

The second task is to build the top-level control unit to select the proper control inputs for the data path. The control unit(Top\_CU) will follow the State Transition Machine(ASM chart) in *Figure 1*, the State Transition Diagram in *Figure 2*, and the Output Table of *Table 3* below.

The next task is to connect the DP and CU module by creating another module called Full\_Calc and further functionally verify it. Specifically, this task provides the proper amount of clock cycle and proper control inputs to the top-level module which would receive only the final result of the operation. The error signal (Err) if the divisor is zero, and the finished signal (done) at the end of the state.

The fourth task is hardware validation the top level FullCalc machine. The clock for this module is a debounce button. The inputs x, y, and f are DIP switches. The current state(CS) and the output result(out) are the seven-segment LED.

*Table 2: List of module for task 4*

Module	Function
<b>FullCalc_FPGA</b>	This is the top-level FPGA hardware module that connects all the necessary module for input switches, buttons, and LEDs.
<b>binary2bcd</b>	This module converts the output result (out) from binary to bcd as ones and tenths value since the maximum result value is 15.
<b>button_debouncer</b>	This module acts as the clock control input
<b>clk_gen</b>	This module produce 5kHz clock signal for the button_debouncer module.
<b>led_mux</b>	This module is taking place in the output of bcd_to_7seg. This module is select the chosen LED to activate.
<b>bcd_to_7seg</b>	This is a decoder module which converts a 4-bit input to 8-bit encoded for the seven-segment display .

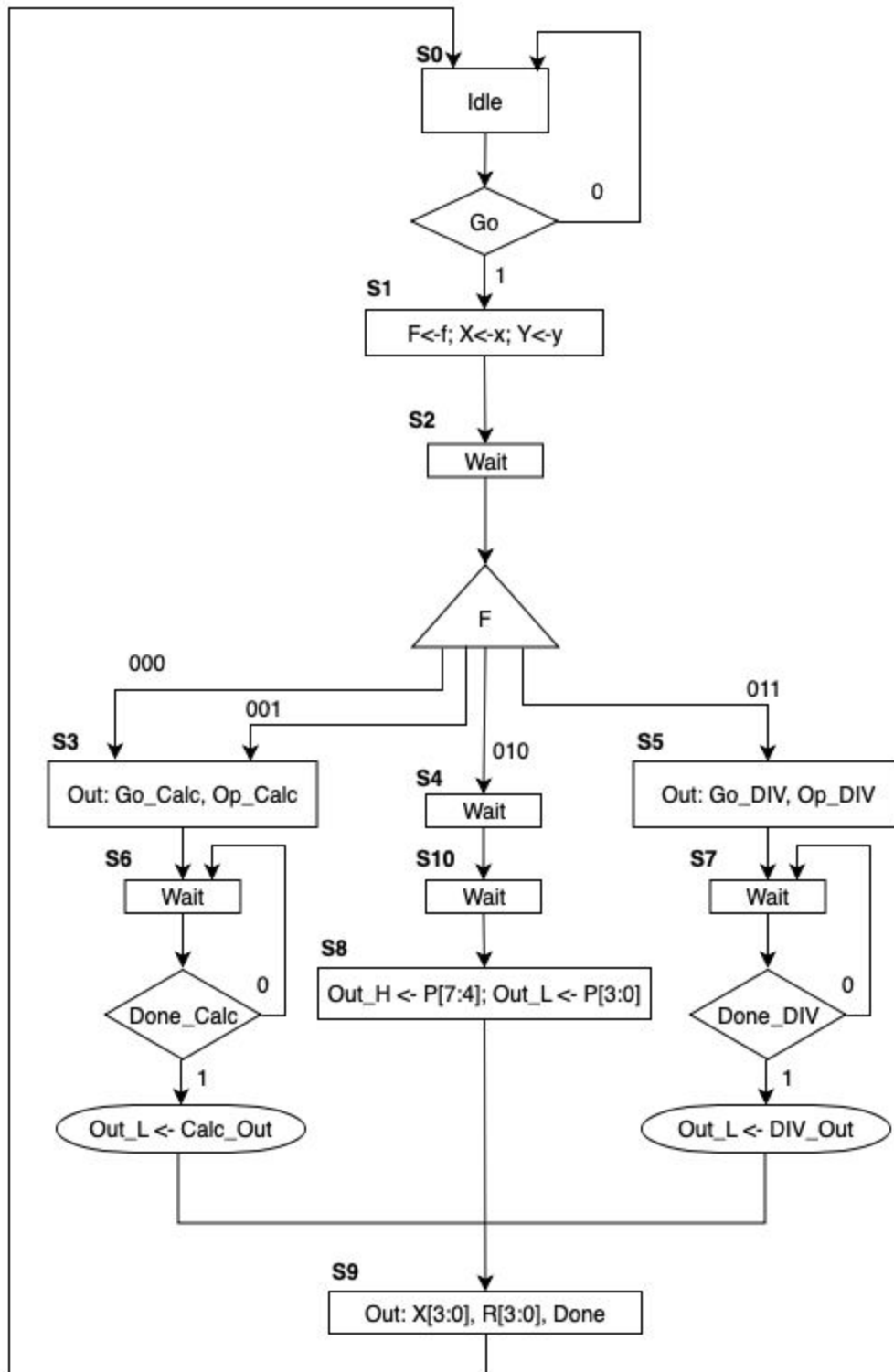


Figure 1: ASM chart describing the Control Unit system's cycle by cycle

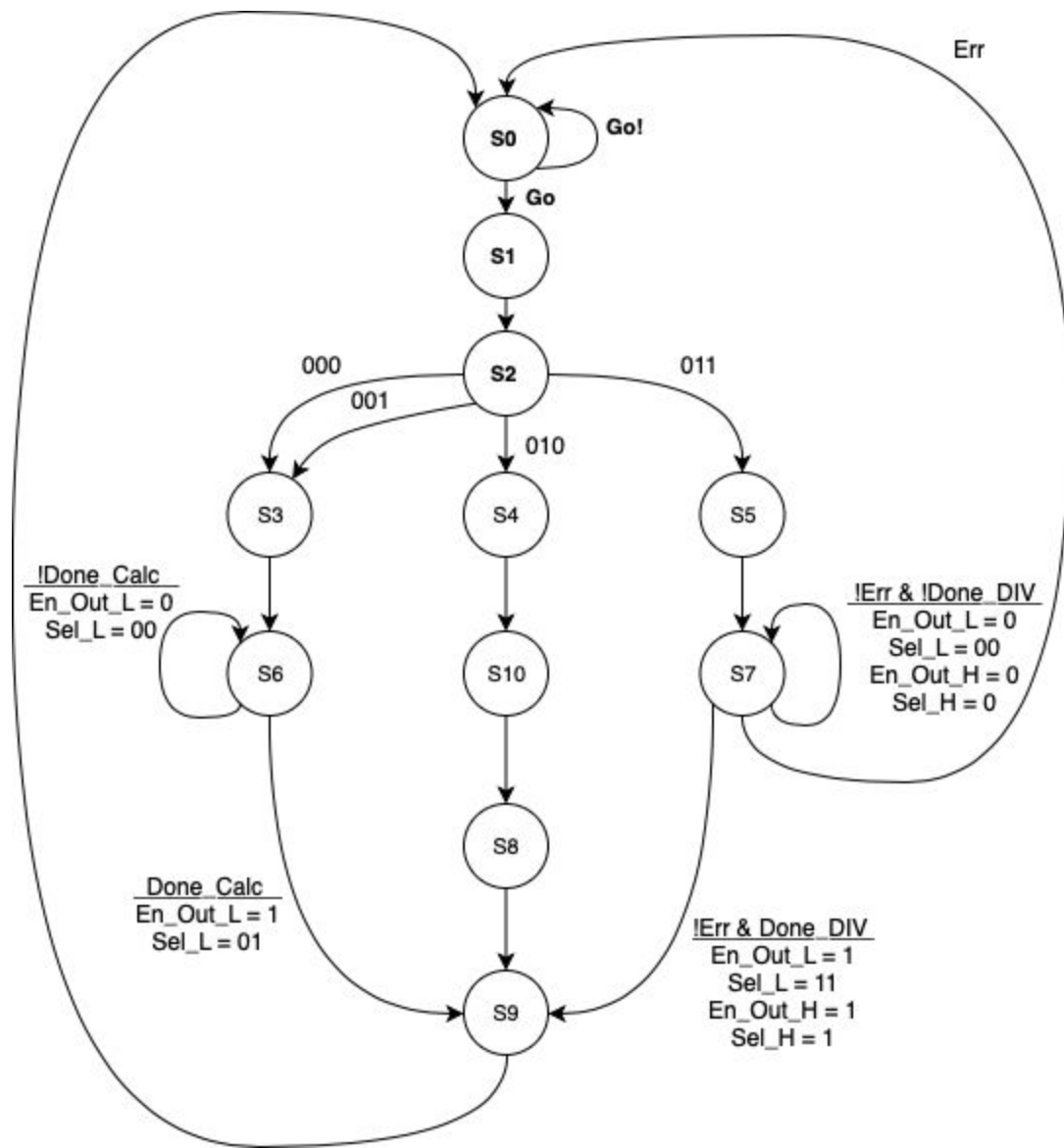


Figure 2: State transition diagram extracted from the ASM chart above

Table 3: Output Logic of the FSM extracted from the ASM chart above

Input				Outputs										
C	F	Don	Don	En	En	En	Go	Go	Op_C	Sel_H	Sel_L	En_Out	En_O	Done
S	[2:0]	e_C	e_D	_F	_X	_Y	_C	_D	alc[1:0]		[1:0]	_H	ut_L	
alc		IV					alc	IV						
S0	000	0	0	0	0	0	0	0	00	0	00	0	0	0
S1	000	0	0	1	1	1	0	0	00	0	00	0	0	0
S2	000	0	0	0	0	0	0	0	00	0	00	0	0	0
S3	000	0	0	0	0	0	1	0	00	0	00	0	0	0
	001	0	0	0	0	0	1	0	01	0	00	0	0	0

S4	000	0	0	0	0	0	0	0	00	0	00	0	0	0
S5	000	0	1	0	0	0	0	0	00	0	00	0	0	0
S6	000	0	0	0	0	0	0	0	00	0	00	0	0	0
	001	0	0	0	0	0	0	0	01	0	00	0	0	0
	000	1	0	0	0	0	0	0	00	0	01	0	1	0
	001	1	0	0	0	0	0	0	01	0	01	0	1	0
S7	000	0	0	0	0	0	0	0	00	0	00	0	0	0
	000	0	1	0	0	0	0	0	00	1	11	1	1	0
S8	00	0	0	0	0	0	0	0	00	0	10	1	1	0
S9	000	0	0	0	0	0	0	0	00	0	00	0	0	1
S10	000	0	0	0	0	0	0	0	00	0	00	0	0	0

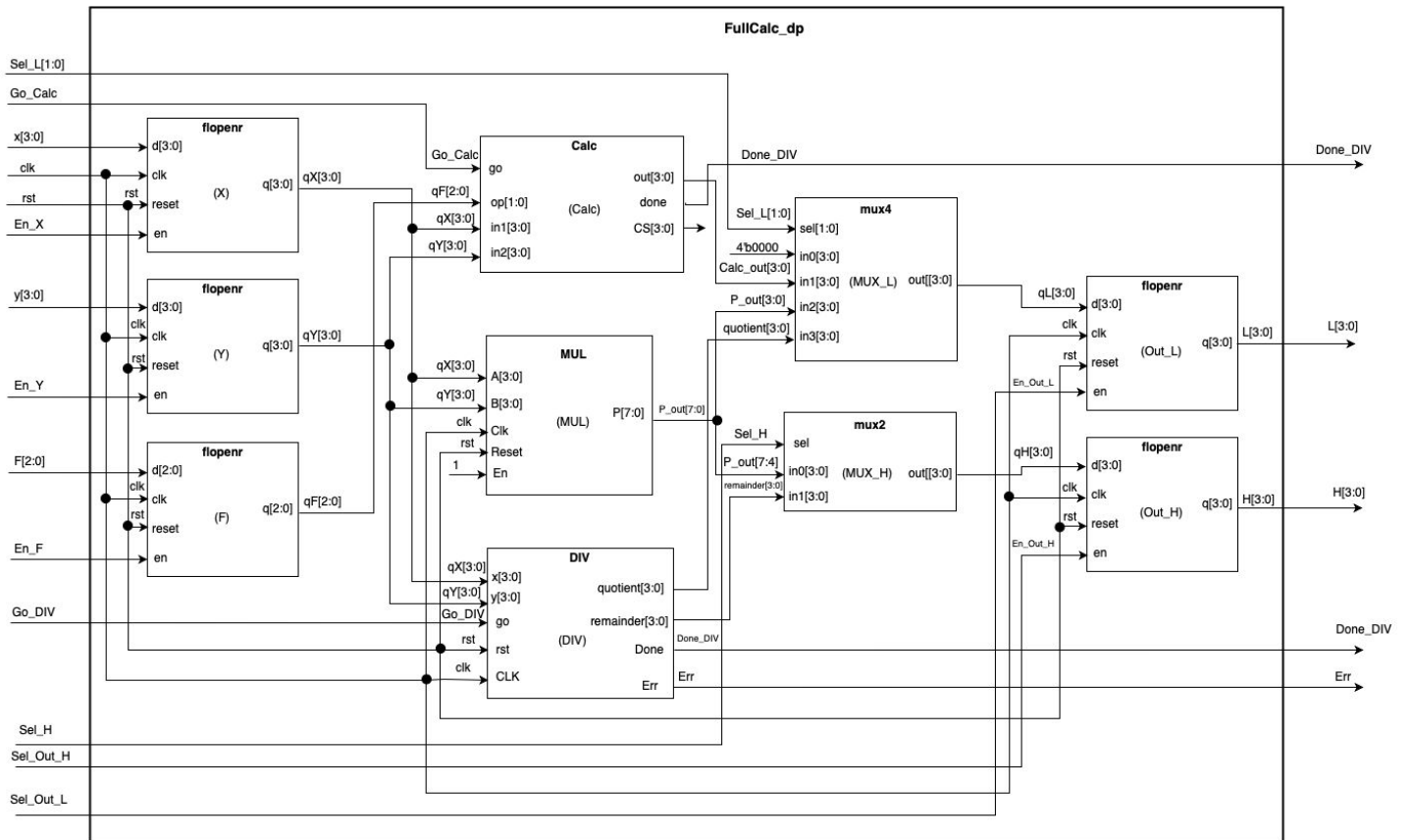


Figure 3: Block diagram of the Data Path for Task 1

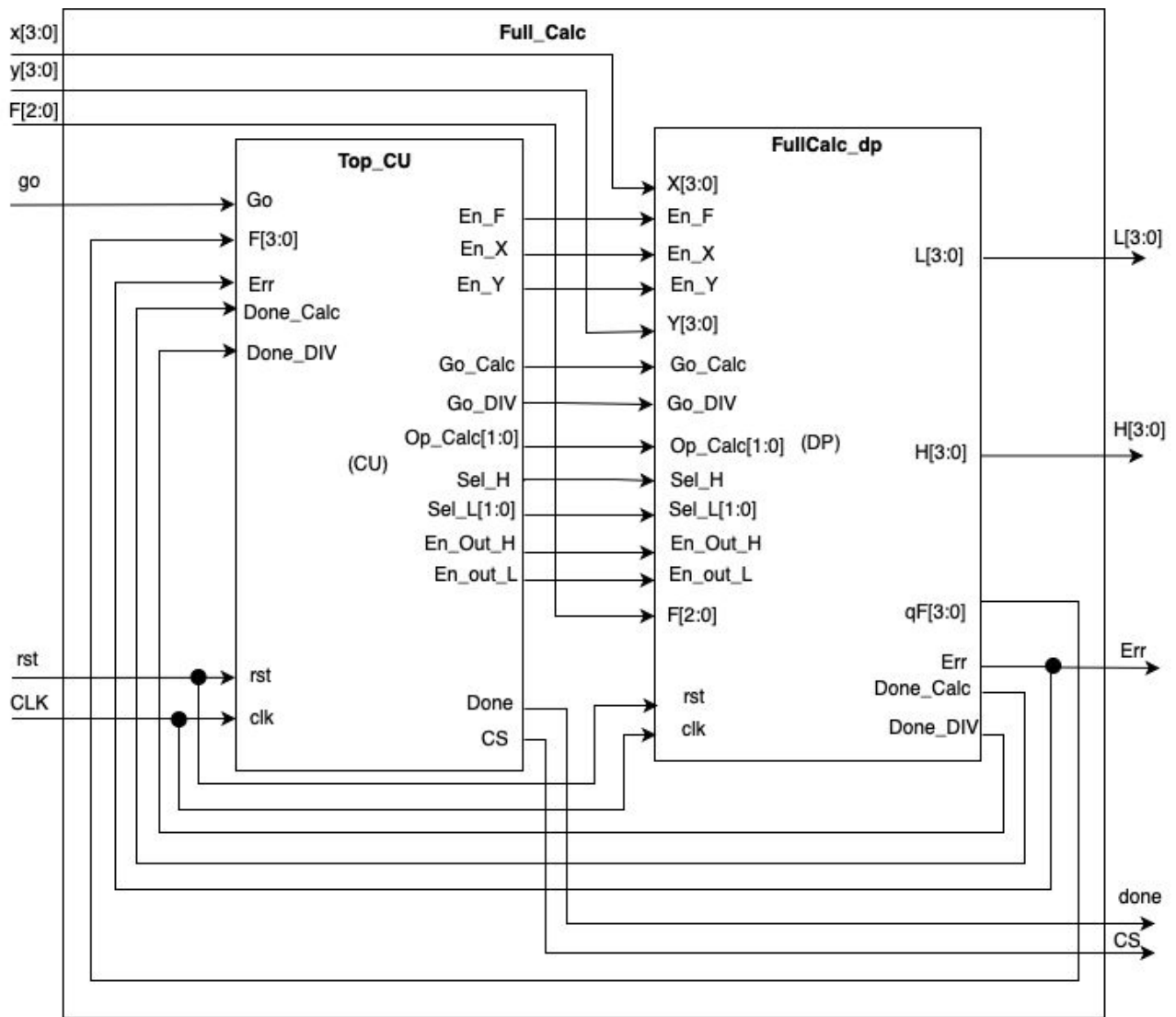


Figure 4: Top level block diagram of the integer divider for Task 3

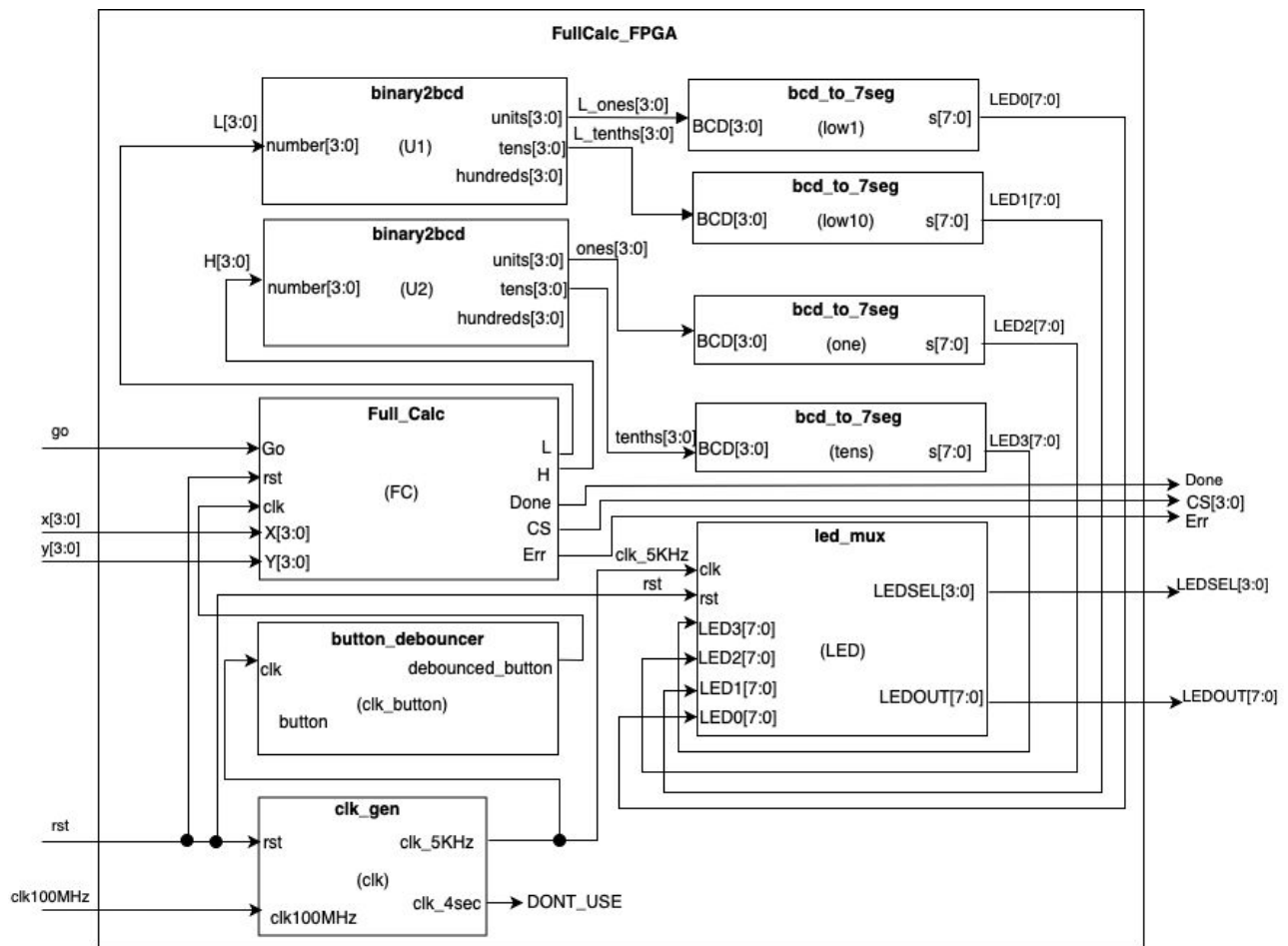


Figure 5: Block diagram of the FPGA hardware validation for Task 4



## Simulation Result

 


Figure 6: Simulation waveforms produced from *FullCalc\_tb.v* testbench file

This testbench went through four operations (addition, subtraction, multiplication, and division). For the division, the simulation also look at the case when the dividend is zero(  $y_{tb} = 0$  ). The operation is considered to be done when the Done\_tb signal is 1 and providing the final result at state S9(  $CS = 9$  ). According to *Figure 6* above, the first operation is addition (  $F_{tb} = 000$  ), the two input operands are 3 and 5 (  $X_{tb} = 3$  and  $Y_{tb} = 5$  ) which give the final result to be 8(  $L_{tb} = 8$  ). The second operation is subtraction (  $F_{tb} = 001$  ), the two input operands are 5 and 3 (  $X_{tb} = 5$  and  $Y_{tb} = 3$  ) which give the final result to be 2(  $L_{tb} = 2$  ). The third operation is multiplication (  $F_{tb} = 010$  ), the two input operands are 5 and 7 (  $X_{tb} = 5$  and  $Y_{tb} = 7$  ) which give the final result to be 35(  $H_{tb} = 2$ ,  $L_{tb} = 3$  in Hex). The last operation is division (  $F_{tb} = 011$  ), the two input operands are 11 and 7 (  $X_{tb} = 11$  and  $Y_{tb} = 7$  ) which give the final result for the quotient to be 1 and the remainder is 3(  $H_{tb} = 3$ ,  $L_{tb} = 1$  ). For the corner case where the operands  $Y_{tb}$  is zero, we can observe that the Err\_tb is 1 at state 7 and then move back to state 0. Since the simulation have provided the waveform as expected, the functional verification process is considered to be successful.

## FPGA Validation

For the FPGA validation process, the rightmost four switches are 4-bit input integer (x), the leftmost four switches are 4-bit integer(y). The center button is the clock, the left button is reset input, and the right button is go input. The 4-bit output(L) need two seven segment LEDs on the left since the maximum value is 15. The 4-bit output(H) need two seven segment LEDs on the right since the maximum value is also 15. There also LED for the Done, Err, and the Current State signals. The done signal should lit at state S9 when the operation is done. The Err signal is On(1) when  $Y=0$  if choosing division operation. According to *Figure 7*, when choosing the addition operation (000) between 0111 and 0010 (7+2), the result appeared in the L seven-segments is 9 which is correct. According to *Figure 8*, when choosing the subtraction operation (001) between 0111 and 0010 (7-2), the result appeared in the L seven-segments is 7 which is also correct. According to *Figure 9*, when choosing the

multiplication operation (010) between 0111 and 0111 ( $7*7$ ), the result appeared in the H seven-segments is 3 and L seven-segments is 1 which is correct because it is 49 in digit and 31 in Hex. According to Figure 10, when choosing the division operation (011) between 0111 and 0111 ( $7/7$ ), the result appeared in the L seven-segments is 1 which is also correct. According to Figure 11, when choosing the division operation (011) between 0111 and 0000 ( $7/0$ ), the Error(Err) signal is ON at state 0111(S7) and then go back to idle state (S0). For this reason, the hardware validation process was successful.

 


Figure 7: 0111 + 0010 ( $7+2$ )



 


Figure 8 : 0111 - 0010 (7-2)

 


Figure 9 : 0111 \* 0111 (7\*7)





## **Conclusion**

Overall, both the simulation and FPGA validation process for all the task was successfully performed since the result is as expected. This lab experiment helps strengthen our knowledge on systematic design by creating ASM chart, Output Logic table, and State Transition Diagram. This lab was a bit challenging since we have to reuse old material built from previous lab instead of design from the ground up. Therefore, additional modification as well as better understanding about the state transitioning is required.

Last but not least, we would like to thank you our TA Nelson Wong and Professor Donald Hung for giving us a very challenging but also fun semester! Thank you for giving more attention in grading the reports as well as explaining the course material. We hope you have an awesome Winter Break and hoping to learn more from you in the future course.

## Appendix

### a. Source Code

#### Task 1

#### FullCalc\_dp.v

```
module FullCalc_dp(input [3:0] x, y,
    input [2:0] f,
    input En_F, En_X, En_Y,
    input Go_Calc, Go_DIV,
    input [1:0] Op_Calc,
    input Sel_H, En_Out_H, En_Out_L, Sel_square,
    input [1:0] Sel_L,
    input rst, clk,
    output Done_Calc, Done_DIV,
    output [2:0] qF,
    output [3:0] L, H,
    output Err
);

wire [3:0] qX, qY, X_square;
wire [3:0] Calc_out, quotient, remainder, qL, qH;
wire [7:0] P_out;

flopnr#3 F( .clk(clk), .reset(rst), .en(En_F), .d(f), .q(qF));
flopnr#4 X( .clk(clk), .reset(rst), .en(En_X), .d(x), .q(qX));
flopnr#4 Y( .clk(clk), .reset(rst), .en(En_Y), .d(y), .q(qY));

mux2 #4 MUX_square(.sel(Sel_square),
    .in0(qY),
    .in1(qX),
    .out(X_square));

Calc Calc(.go(Go_Calc),
    .op(Op_Calc),
    .in1(qX),
    .in2(qY),
    .done(Done_Calc),
    .clk(clk),
    //.CS(),
    .out(Calc_out));

MUL MUL(.A(qX),
    .B(X_square),
    .P(P_out),
    .Clk(clk),
    .Reset(rst),
    .En(1));

DIV DIV(.x(qX),
    .y(qY),
    .go(Go_DIV),
    .rst(rst),
    .CLK(clk),
    .quotient(quotient),
    .remainder(remainder),
    .Err(Err),
    .Done(Done_DIV));

mux4 #4 MUX_L(.sel(Sel_L),
```

```

        .in0(4'b0000),
        .in1(Calc_out),
        .in2(P_out[3:0]),
        .in3(quotient),
        .out(qL));

mux2 #4 MUX_H(.sel(Sel_H),
        .in0(P_out[7:4]),
        .in1(remainder),
        .out(qH));

flopnr#4 Out_H( .clk(clk), .reset(rst), .en(En_Out_H), .d(qH), .q(H));
flopnr#4 Out_L( .clk(clk), .reset(rst), .en(En_Out_L), .d(qL), .q(L));

endmodule

```

## Top\_CU.v

```

module Top_CU(input Go,
        input [2:0] F,
        input clk, rst,
        input Done_Calc,
        input Done_DIV,
        output reg Sel_square,
        output reg En_F,
        output reg En_X,
        output reg En_Y,
        output reg Go_Calc,
        output reg Go_DIV,
        output reg [1:0] Op_Calc,
        output reg Sel_H,
        output reg [1:0] Sel_L,
        output reg En_Out_H,
        output reg En_Out_L,
        output reg Done,
        output reg [3:0] CS,
        input Err
);

parameter S0 = 4'b0000,
        S1 = 4'b0001,
        S2 = 4'b0010,
        S3 = 4'b0011,
        S4 = 4'b0100,
        S5 = 4'b0101,
        S6 = 4'b0110,
        S7 = 4'b0111,
        S8 = 4'b1000,
        S9 = 4'b1001,
        S10 = 4'b1010;

reg [3:0] NS;

always@(CS, Go, F, Done_Calc, Done_DIV, Err)
begin
    case(CS)
        S0:
            begin
                NS = S1;

```

```

        if(!Go) NS = S0;
        else NS = S1;
    end

S1:
begin
    NS = S2;
end

S2:
begin
    if (F == 3'b000) NS = S3;//add
    else if (F == 3'b001) NS = S3;//sub
    else if (F == 3'b010) NS = S4;//mul
    else if (F == 3'b011) NS = S5;//div
    else if (F == 3'b100) NS = S3;//+1
    else if (F == 3'b101) NS = S3;//-1
    else if (F == 3'b110) NS = S4;//square
end

S3://small calc state
begin
    NS = S6;

end

S4://mult state
begin
    NS = S10;
end

S5://DIV state
begin
    NS = S7;
end

S6://small calc clock state
begin
    if (!Done_Calc) NS = S6;// loop back to this state if
Done_Calc is not on
    else NS = S9; //If not, move to done state
end

S10:
begin
    NS = S8;
end

S8:
begin
    NS = S9;//done state
end

S7://DIV state
begin
    if(Err) NS = S0;
    else begin
        if (!Done_DIV) NS = S7;
        else NS = S9; //done state
    end
end

S9:

```



```

        begin
            NS = S0;
        end

        default:
        begin
            NS = S0;
        end
    endcase
end

always@(posedge clk, posedge rst)
begin
    if(rst) CS = S0;
    else CS <= NS;
end

always@(CS, F, Done_Calc, Done_DIV)
begin
    case(CS)
    S0://idle
    begin
        En_F = 0;
        En_X = 0;
        En_Y = 0;
        Go_Calc = 0;
        Go_DIV = 0;
        Op_Calc = 2'b00;
        Sel_H = 0;
        Sel_L = 2'b00;
        En_Out_H = 0;
        En_Out_L = 0;
        Done = 0;
    end

    S1://load state
    begin
        En_F = 1;// load F
        En_X = 1;// load X
        En_Y = 1;// load Y
        Go_Calc = 0;
        Go_DIV = 0;
        Op_Calc = 2'b00;
        Sel_H = 0;
        Sel_L = 2'b00;
        En_Out_H = 0;
        En_Out_L = 0;
        Done = 0;
    end

    S2://wait state
    begin
        En_F = 0;// load F
        En_X = 0;// load X
        En_Y = 0;// load Y
        Go_Calc = 0;
        Go_DIV = 0;
        //Op_Calc = 2'b00;
        Sel_H = 0;
        Sel_L = 2'b00;
        En_Out_H = 0;
    end
    end

```

```

        En_Out_L = 0;
        Done = 0;
        Sel_square = 0;

        if(F == 3'b000)
        begin
            Op_Calc = 2'b00;//add
        end

        else if(F == 3'b001)
        begin
            Op_Calc = 2'b01;//sub
        end

        else if(F == 3'b100)
        begin
            Op_Calc = 2'b01;//+1
        end

        else if(F == 3'b101)
        begin
            Op_Calc = 2'b01;//-1
        end

    end

S3://small Calc state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 1;//enable small calc module
    Go_DIV = 0;
    //Op_Calc = 2'b00;
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 0;
    Sel_square = 0;

    if(F == 3'b000)
    begin
        Op_Calc = 2'b00;//add
    end

    else if(F == 3'b001)
    begin
        Op_Calc = 2'b01;//sub
    end

    else if(F == 3'b100)
    begin
        Op_Calc = 2'b01;//+1
    end

    else if(F == 3'b101)
    begin
        Op_Calc = 2'b01;//-1
    end
end

```

```

end

S6://load output state when done . If not, loop again in this state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;
    Sel_H = 0;
    //Sel_L = 2'b00;
    En_Out_H = 0;//keep the output 0 for the small calc state
    //En_out_L = 0;
    Sel_square = 0;
    Done = 0;
    if(!Done_Calc)
    begin
        Sel_L = 2'b00;
        En_Out_L = 0;
    end
    else
    begin
        Sel_L = 2'b01;
        En_Out_L = 1;
    end

    if(F == 3'b000)
    begin
        Op_Calc = 2'b00;//add
    end

    else if(F == 3'b001)
    begin
        Op_Calc = 2'b01;//sub
    end

    else if(F == 3'b100)
    begin
        Op_Calc = 2'b01;//+1
    end

    else if(F == 3'b101)
    begin
        Op_Calc = 2'b01;//-1
    end

end

S4://wait state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;

```

```

        Done = 0;

end

S10://wait state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 0;
    Go_DIV = 0;
    //Op_Calc = 2'b00;
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 0;
    Sel_square = 0;

end

S8://load MUL result state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;//dont care
    Sel_H = 0;//selec P high
    Sel_L = 2'b10;//selec P Low
    En_Out_H = 1;
    En_Out_L = 1;
    Done = 0;

end

S5://load DIV result state
begin
    En_F = 0;// load F
    En_X = 0;// load X
    En_Y = 0;// load Y
    Go_Calc = 0;
    Go_DIV = 1;
    Op_Calc = 2'b00;//dont care
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 0;
    Sel_square = 0;

end

S7://wait state
begin

```

```

    En_F = 0; // load F
    En_X = 0; // load X
    En_Y = 0; // load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;
    //Sel_H = 0;
    //Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 0;

    if(!Done_DIV)
    begin
        Sel_L = 2'b00;
        Sel_H = 0;
        En_Out_H = 0;
        En_Out_L = 0;
    end
    else //if Done_Div is on output the result
    begin
        Sel_L = 2'b11; //pick quotient
        Sel_H = 1; //pick remainder
        En_Out_H = 1; //output the quotient
        En_Out_L = 1; //output the remainder
    end
end

S9:
begin
    En_F = 0; // load F
    En_X = 0; // load X
    En_Y = 0; // load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 1;
    Sel_square = 0;
end

default: // just like wait state /do nothing
begin
    En_F = 0; // load F
    En_X = 0; // load X
    En_Y = 0; // load Y
    Go_Calc = 0;
    Go_DIV = 0;
    Op_Calc = 2'b00;
    Sel_H = 0;
    Sel_L = 2'b00;
    En_Out_H = 0;
    En_Out_L = 0;
    Done = 0;
    Sel_square = 0;
    if(F == 3'b000)
    begin
        Op_Calc = 2'b00; //add
    end
end

```

```

        else if(F == 3'b001)
        begin
            Op_Calc = 2'b01;//sub
        end

        else if(F == 3'b100)
        begin
            Op_Calc = 2'b01;//+1
        end

        else if(F == 3'b101)
        begin
            Op_Calc = 2'b01;//-1
        end
    end

endcase

end

endmodule

```

### **flopenr.v**

```

module flopenr#(parameter WIDTH = 8)
    (input  clk, reset,
     input  en,
     input  [WIDTH-1:0] d,
     output reg[WIDTH-1:0] q
    );
    always@(posedge clk, posedge reset)
        if (reset)q<=0;
        else if(en) q<=d;
        else q<=q;
endmodule

```

### **mux2.v**

```

module mux2 #(WIDTH = 5) (
    input  wire      sel,
    input  wire [WIDTH-1:0] in0,
    input  wire [WIDTH-1:0] in1,
    output wire [WIDTH-1:0] out
);

    assign out = (sel == 1'b1) ? in1 : in0;

endmodule

```

### **mux4.v**

```

module mux4 #(parameter WIDTH = 4) (
    input  wire [1:0]      sel,
    input  wire [WIDTH-1:0] in0,
    input  wire [WIDTH-1:0] in1,
    input  wire [WIDTH-1:0] in2,
    input  wire [WIDTH-1:0] in3,
    output reg  [WIDTH-1:0] out
);

always @ (*) begin
    case(sel)
        2'b00: out = in0;
        2'b01: out = in1;
        2'b10: out = in2;
        2'b11: out = in3;
    endcase
end

endmodule

```

## Calc.v

```

module Calc(input go,
             input [1:0] op,
             input clk,
             input [3:0] in1,in2,
             output [3:0] CS,
             output done,
             output [3:0] out
);

wire [1:0] s1, wa, c, raa, rab;
wire we, rea, reb, s2;

cu cu(.go(go),
     .op(op),
     .clk(clk),
     .done(done),
     .CS(CS),
     .s1(s1),
     .wa(wa),
     .c(c),
     .raa(raa),
     .rab(rab),
     .we(we),
     .rea(rea),
     .reb(reb),
     .s2(s2));

small_calculator_dp DP(.clk(clk),
                       .in1(in1),
                       .in2(in2),
                       .s1(s1),
                       .wa(wa),
                       .raa(raa),
                       .rab(rab),
                       .c(c),
                       .we(we),
                       .rea(rea),
                       .reb(reb),

```

```

        .s2(s2),
        .out(out));

endmodule

```

## MUL.v

```

module MUL( input [3:0]A, input[3:0]B, output[7:0]P,
            input Clk,input Reset, input En);
    wire[3:0] pp3,pp2, pp1, pp0;
    wire[3:0] q_A, q_B;
    wire[7:0] q_top, q_bottom, d_P;
    wire[7:0] shifted_3, shifted_2, shifted_1, shifted_0;
    wire[7:0] top, bottom, mid;
    wire Cout_top_left, Cout_top_right, Cout_bottom_left, Cout_bottom_right,
    Cout_mid_left, Cout_mid_right;

    // insert input registers to the inputs
    flopenr#4 A_reg( .clk(Clk), .reset(Reset), .en(En), .d(A), .q(q_A));
    flopenr#4 B_reg( .clk(Clk), .reset(Reset), .en(En), .d(B), .q(q_B));
    // use to and for the function (a3a2a1a0)*bi
    AND and_3(.A(q_A[3:0]), .B(q_B[3]), .out(pp3[3:0]));
    AND and_2(.A(q_A[3:0]), .B(q_B[2]), .out(pp2[3:0]));
    AND and_1(.A(q_A[3:0]), .B(q_B[1]), .out(pp1[3:0]));
    AND and_0(.A(q_A[3:0]), .B(q_B[0]), .out(pp0[3:0]));

    //shift every pp by +1 bit
    shift shift_3(.pp(pp3[3:0]), .index(2'b11), .out(shifted_3));
    shift shift_2(.pp(pp2[3:0]), .index(2'b10), .out(shifted_2));
    shift shift_1(.pp(pp1[3:0]), .index(2'b01), .out(shifted_1));
    shift shift_0(.pp(pp0[3:0]), .index(2'b00), .out(shifted_0));

    //add all 4 together
    //top
    CLA top_right(.A_1(shifted_0[3:0]), .B_1(shifted_1[3:0]), .Cin(1'b0),
    .sum(top[3:0]), .Cout(Cout_top_right));
    CLA top_left(.A_1(shifted_0[7:4]), .B_1(shifted_1[7:4]), .Cin(Cout_top_right),
    .sum(top[7:4]), .Cout(Cout_top_left));
    //bottom
    CLA bottom_right(.A_1(shifted_2[3:0]), .B_1(shifted_3[3:0]), .Cin(1'b0),
    .sum(bottom[3:0]), .Cout(Cout_bottom_right));
    CLA bottom_left(.A_1(shifted_2[7:4]), .B_1(shifted_3[7:4]),
    .Cin(Cout_bottom_right),
    .sum(bottom[7:4]), .Cout(Cout_bottom_left));
    //insert stage registers
    flopenr top_reg( .clk(Clk), .reset(Reset), .en(En), .d(top), .q(q_top));
    flopenr bottom_reg(.clk(Clk), .reset(Reset), .en(En), .d(bottom),
    .q(q_bottom));
    //add top and bottom together
    CLA mid_right(.A_1(q_top[3:0]), .B_1(q_bottom[3:0]), .Cin(1'b0),
    .sum(d_P[3:0]), .Cout(Cout_mid_right));
    CLA mid_left(.A_1(q_top[7:4]), .B_1(q_bottom[7:4]), .Cin(Cout_mid_right),
    .sum(d_P[7:4]), .Cout(Cout_mid_left));
    ///insert output registers
    flopenr out_reg( .clk(Clk), .reset(Reset), .en(En), .d(d_P), .q(P));

endmodule

```



## DIV.v

```
module DIV(input [3:0] x,
           input [3:0] y,
           input go,
           input rst,
           input CLK,
           output [3:0] quotient,
           output [3:0] remainder,
           output Done, Err);

    wire yZero, cnt, R_lt_Y;
    wire x_RightIn, x_LD, x_SL, y_LD, r_LD, r_SL, r_SR;
    wire s1,s2,s3;
    wire [3:0] n;
    wire cnt_LD, cnt_en;
    ControlUnit FSM (.Go(go),
                    .clk(CLK),
                    .rst(rst),
                    .yZero(yZero),
                    .cnt(cnt),
                    .R_lt_Y(R_lt_Y),
                    .x_RightIn(x_RightIn),
                    .x_LD(x_LD),
                    .x_SL(x_SL),
                    .y_LD(y_LD),
                    .r_LD(r_LD),
                    .r_SL(r_SL),
                    .r_SR(r_SR),
                    .s1(s1),
                    .s2(s2),
                    .s3(s3),
                    .n(n),
                    .cnt_LD(cnt_LD),
                    .cnt_en(cnt_en),
                    .Done(Done),
                    .Err(Err));
    data_path DP (.x(x),
                 .x_RightIn(x_RightIn),
                 .x_LD(x_LD),
                 .x_SL(x_SL),
                 .y(y),
                 .y_LD(y_LD),
                 .r_LD(r_LD),
                 .r_SL(r_SL),
                 .r_SR(r_SR),
                 .s1(s1),
                 .s2(s2),
                 .s3(s3),
                 .n(n),
                 .cnt_LD(cnt_LD),
                 .cnt_en(cnt_en),
                 .rst(rst),
                 .clk(CLK),
                 .cnt_out(cnt),
                 .R_lt_Y(R_lt_Y),
                 .yZero(yZero),
                 .Q(quotient),
                 .R(remainder));

endmodule
```

## FullCalc\_FPGA.v

```
module FullCalc_FPGA(input wire go, rst, clkBut, clk100MHz,
    input wire [3:0] x, y,
    input wire [2:0] F,
    output wire done,
    output wire [3:0] CS,
    output wire [3:0] LEDSEL,
    output wire [7:0] LEDOUT,
    output wire Err);

wire DONT_USE;
wire DONT_CARE, dont_use, dont_care;
wire clk_5KHz;
wire debounced_clk;
wire [3:0] L_tenths, L_ones, ones, tenths, H, L,r;
wire [7:0] LED3, LED2, LED1, LED0;

clk_gen      clk(.clk100MHz(clk100MHz),
    .rst(rst),
    .clk_4sec(DONT_USE),
    .clk_5KHz(clk_5KHz));

button_debouncer  clk_button(.clk(clk_5KHz),
    .button(clkBut),
    .debounced_button(debounced_clk));

Full_Calc      FC(.Go(go),
    .X(x),
    .Y(y),
    .F(F),
    .clk(debounced_clk),
    .rst(rst),
    .Done(done),
    .H(H),
    .L(L),
    .CS(CS),
    .Err(Err));

binary2bcd U1      (.number(L),
    .units(ones),
    .tens(tenths),
    .hundreds(DONT_CARE));

binary2bcd U2      (.number(H),
    .units(L_ones),
    .tens(L_tenths),
    .hundreds(dont_care));

bcd_to_7seg      low1 (.BCD(L_ones),
    .s(LED2));
bcd_to_7seg      low10 (.BCD(L_tenths),
    .s(LED3));
bcd_to_7seg      tens(.BCD(tenths),
    .s(LED1));
bcd_to_7seg      one(.BCD(ones),
    .s(LED0));

led_mux          LED(.clk(clk_5KHz),
```

```

        .rst(rst),
        .LED3(LED3),
        .LED2(LED2),
        .LED1(LED1),
        .LED0(LED0),
        .LEDSEL(LEDSEL),
        .LEDOUT(LEDOUT));
endmodule

```

## FullCalc\_tb.v

```

module FullCalc_tb;
    reg Go_tb;
    reg [3:0] X_tb, Y_tb;
    reg [2:0] F_tb;
    reg clk_tb, rst_tb;
    wire Done_tb;
    wire [3:0] H_tb, L_tb, CS_tb;

    Full_Calc DUT (.Go(Go_tb),
        .X(X_tb),
        .Y(Y_tb),
        .F(F_tb),
        .clk(clk_tb),
        .rst(rst_tb),
        .Done(Done_tb),
        .H(H_tb),
        .L(L_tb),
        .CS(CS_tb));

    task ticktock;
    begin
        #5 clk_tb = ~clk_tb;
        #5 clk_tb = ~clk_tb;
    end
endtask

integer errors;
initial begin
    Go_tb = 0;
    X_tb = 4'b0000;
    Y_tb = 4'b0000;
    F_tb = 3'b000;
    clk_tb = 0;
    rst_tb = 1;

    ticktock();
    ticktock();

    //begin addition
    Go_tb = 1;
    X_tb = 3;
    Y_tb = 5;
    F_tb = 3'b000;
    clk_tb = 0;
    rst_tb = 0;
    ticktock();
    ticktock();
    ticktock();

```

[illegible]

```

        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();
        ticktock();

    end

endmodule

```

## clk\_gen.v

```

module clk_gen (
    input wire clk100MHz,
    input wire rst,
    output reg clk_4sec,
    output reg clk_5KHz
);

integer count1, count2;

always @ (posedge clk100MHz) begin
    if (rst) begin
        count1 = 0;
        count2 = 0;
        clk_5KHz = 0;
        clk_4sec = 0;
    end
    else begin
        if (count1 == 200000000) begin
            clk_4sec = ~clk_4sec;
            count1 = 0;
        end

        if (count2 == 10000) begin
            clk_5KHz = ~clk_5KHz;
            count2 = 0;
        end

        count1 = count1 + 1;
        count2 = count2 + 1;
    end
end

endmodule

```

## button\_debouncer.v

```
module button_debouncer #(parameter depth = 16) (  
    input wire clk,                /* 5 KHz clock */  
    input wire button,             /* Input button from constraints */  
    output reg debounced_button  
);  
  
localparam history_max = (2**depth)-1;  
  
/* History of sampled input button */  
reg [depth-1:0] history;  
  
always @ (posedge clk) begin  
    /* Move history back one sample and insert new sample */  
    history <= { button, history[depth-1:1] };  
  
    /* Assert debounced button if it has been in a consistent state  
throughout history */  
    debounced_button <= (history == history_max) ? 1'b1 : 1'b0;  
end  
  
endmodule
```

## binary2bcd.v

```
module binary2bcd(number, hundreds, tens, units);  
    // I/O Signal Definitions  
    input [3:0] number;  
    output reg [3:0] hundreds;  
    output reg [3:0] tens;  
    output reg [3:0] units;  
  
    // Internal variable for storing bits  
    reg [19:0] shift;  
    integer i;  
  
    always @(number)  
    begin  
        // Clear previous number and store new number in shift register  
        shift[19:8] = 0;  
        shift[7:0] = number;  
  
        // Loop eight times  
        for (i=0; i<8; i=i+1) begin  
            if (shift[11:8] >= 5)  
                shift[11:8] = shift[11:8] + 3;  
  
            if (shift[15:12] >= 5)  
                shift[15:12] = shift[15:12] + 3;  
  
            if (shift[19:16] >= 5)  
                shift[19:16] = shift[19:16] + 3;
```

```

        // Shift entire register left once
        shift = shift << 1;
    end

    // Push decimal numbers to output
    hundreds = shift[19:16];
    tens      = shift[15:12];
    units     = shift[11:8];
end

endmodule

```

## bcd\_to\_7seg.v

```

module bcd_to_7seg (
    input wire [3:0] BCD,
    output reg [7:0] s
);
always @ (BCD) begin
    case (BCD)
        4'd0: s = 8'b11000000;
        4'd1: s = 8'b11111001;
        4'd2: s = 8'b10100100;
        4'd3: s = 8'b10110000;
        4'd4: s = 8'b10011001;
        4'd5: s = 8'b10010010;
        4'd6: s = 8'b10000010;
        4'd7: s = 8'b11111000;
        4'd8: s = 8'b10000000;
        4'd9: s = 8'b10010000;
        default: s = 8'b01111111;
    endcase
end
endmodule

```

## led\_mux.v

```

module led_mux (
    input wire clk,
    input wire rst,
    input wire [7:0] LED3,
    input wire [7:0] LED2,
    input wire [7:0] LED1,
    input wire [7:0] LED0,
    output wire [3:0] LEDSEL,
    output wire [7:0] LEDOUT
);
reg [1:0] index;
reg [11:0] led_ctrl;
assign {LEDSEL, LEDOUT} = led_ctrl;
always @ (posedge clk) index <= (rst) ? 2'b0 : (index + 2'd1);
always @ (index, LED0, LED1, LED2, LED3) begin
    case (index)
        4'd0: led_ctrl <= {4'b1110, LED0};
        4'd1: led_ctrl <= {4'b1101, LED1};
        4'd2: led_ctrl <= {4'b1011, LED2};
    endcase
end

```

```

4'd3: led_ctrl <= {4'b0111, LED3};
default: led_ctrl <= {8'b1111, 8'hFF};
endcase
end
endmodule

```

## FullCalc\_constraints.xdc

```

# Clock signal
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports
{clk100MHz}];
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports
{clk100MHz}];

# input switches
#input1
set_property -dict {PACKAGE_PIN V17 IOSTANDARD LVCMOS33} [get_ports {x[0]}];
set_property -dict {PACKAGE_PIN V16 IOSTANDARD LVCMOS33} [get_ports {x[1]}];
set_property -dict {PACKAGE_PIN W16 IOSTANDARD LVCMOS33} [get_ports {x[2]}];
set_property -dict {PACKAGE_PIN W17 IOSTANDARD LVCMOS33} [get_ports {x[3]}];
#input2
set_property -dict {PACKAGE_PIN W2 IOSTANDARD LVCMOS33} [get_ports {y[0]}];
set_property -dict {PACKAGE_PIN U1 IOSTANDARD LVCMOS33} [get_ports {y[1]}];
set_property -dict {PACKAGE_PIN T1 IOSTANDARD LVCMOS33} [get_ports {y[2]}];
set_property -dict {PACKAGE_PIN R2 IOSTANDARD LVCMOS33} [get_ports {y[3]}];

#inputF
set_property -dict {PACKAGE_PIN W14 IOSTANDARD LVCMOS33} [get_ports {F[0]}];
set_property -dict {PACKAGE_PIN W13 IOSTANDARD LVCMOS33} [get_ports {F[1]}];
set_property -dict {PACKAGE_PIN V2 IOSTANDARD LVCMOS33} [get_ports {F[2]}];

#clock button
set_property -dict {PACKAGE_PIN U18 IOSTANDARD LVCMOS33} [get_ports
{clkBut}];
#go button
set_property -dict {PACKAGE_PIN T17 IOSTANDARD LVCMOS33} [get_ports {go}];
#reset button
set_property -dict {PACKAGE_PIN W19 IOSTANDARD LVCMOS33} [get_ports {rst}];

# output LED
set_property -dict {PACKAGE_PIN L1 IOSTANDARD LVCMOS33} [get_ports {done}];

# output Err
set_property -dict {PACKAGE_PIN P1 IOSTANDARD LVCMOS33} [get_ports {Err}];

# output CS
set_property -dict {PACKAGE_PIN W3 IOSTANDARD LVCMOS33} [get_ports {CS[0]}];
set_property -dict {PACKAGE_PIN U3 IOSTANDARD LVCMOS33} [get_ports {CS[1]}];
set_property -dict {PACKAGE_PIN P3 IOSTANDARD LVCMOS33} [get_ports {CS[2]}];
set_property -dict {PACKAGE_PIN N3 IOSTANDARD LVCMOS33} [get_ports {CS[3]}];

#LED selection
set_property -dict {PACKAGE_PIN U2 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[0]}]; # AN0
set_property -dict {PACKAGE_PIN U4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[1]}]; # AN1

```



```

set_property -dict {PACKAGE_PIN V4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[2]}}; # AN2
set_property -dict {PACKAGE_PIN W4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[3]}}; # AN3

#LED output
set_property -dict {PACKAGE_PIN W7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[0]}}; # CA
set_property -dict {PACKAGE_PIN W6 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[1]}}; # CB
set_property -dict {PACKAGE_PIN U8 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[2]}}; # CC
set_property -dict {PACKAGE_PIN V8 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[3]}}; # CD
set_property -dict {PACKAGE_PIN U5 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[4]}}; # CE
set_property -dict {PACKAGE_PIN V5 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[5]}}; # CF
set_property -dict {PACKAGE_PIN U7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[6]}}; # CG
set_property -dict {PACKAGE_PIN V7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[7]}}; # DP

```