

San Jose State University  
Department of Computer Engineering

CMPE 125 Lab Report

Lab 7 Report

Title System-level Design (1): The Small Calculator

Semester FALL 2019

Date 10-28-19

by

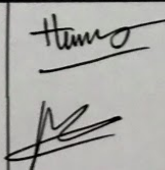
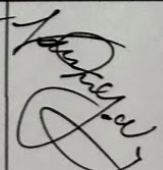
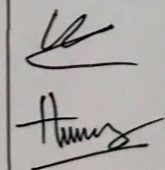
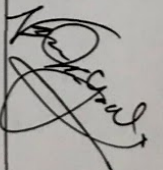
Name HUNG NGUYEN  
(typed)

SID 012392081  
(typed)

Name PHAT LE  
(typed)

SID 012067666  
(typed)

Lab Checkup Record

Week	Performed By (signature)	Checked By (signature)	Tasks Successfully Completed*	Tasks Partially Completed*	Tasks Failed or Not Performed*
1			100%		
2			100%		

\* Detailed descriptions must be given in the report.

## Introduction

The purpose of this lab is to become familiar with system-level design methodologies, with an emphasis on the control portion, and with the procedure and tools for system-level development. Specifically, the main task is to design, functionally verify, and FPGA hardware validation a small calculator system that requires a Control Unit to control signals of a simple computation system called Data Path.

## Design Methodology

The first task is to functionally verify the provided module named Data Path(DP). The DP is the top-level module that connects a 4 to 1 mux, a register file, an alu, and a 2 to 1 mux. Its main functionality is to take in two 4-bit inputs and store them in the register file cycle by cycle. The DP then performs the operation based on a control signal (+,-,&^) and store the result in the register file for the next clock cycle. Lastly, it outputs the result by another clock cycle.

*Table 1: List of modules for Task 1*

Module	Function
<b>small_calculator_dp</b>	This is the top-level module of the data-path which connects four modules below.
<b>mux4</b>	This module selects the kind of inputs to go into the system such as input1(in1), input2(in2), and the result.
<b>register_file</b>	This module receives the selected input from the mux4 module and stores it in the register file. After it stored input1 and 2 in the register, the module would read both inputs at outputs raa and rab so the alu can process the result. The result from the two inputs then is stored at the register file and being read out from both output raa and rab.
<b>alu</b>	This module selects the appropriate operations based on the outputs from the register_file module. When the register file read outputs are the data from input 1 and 2, the alu would generate the result based on the operation selection(+,-,&^). When the register file read outputs are the same value of the result, the alu module then selects and operation(&) to pass the result to the mux2 module below.

<b>mux2</b>	This module only selects the final result passing by the alu module. It then outputs the result and reaches the end of the data path.
<b>small_calculator_dp_tb</b>	This module manually decides the appropriate inputs for the DataPath module and verify whether the functionality of the DataPath is correct.

The second task of the lab is to design, functionally verify the control unit (CU) which is a finite state machine (FSM). The functionality of this control unit is to provide proper output signals for the input controls of the data path module based on the 2-bit operation selection input(+,-,&,<sup>^</sup>), the begin signal is toggled (go input). Furthermore, the CU would output the current state and turn ON the done signal(1) in the last state.

*Table 2 : List of module for task 2*

Module	Function
<b>cu</b>	This is control unit module. It acts like a controller which is pass control signal to the datapath based on each stage.
<b>cu_tb</b>	This is the testbench module which tests all possible operation inputs for the same amount of clock toggle transitional state.

The third task is to connect the DP and CU module by creating another module call calculator and further functionally verify it. Similar to the input of task 1 and 2, this task provides the same amount of clock cycle and proper inputs to the top level module which would receive only the final result of the operation, the current state(CS), and the finished signal (done) at the end of the state.

*Table 3: List of module for task 3*

Module	Function
<b>calculator</b>	This is a top-level module of calculator. It will contain both control-unit module and datapath module.
<b>calculator_tb</b>	This is calculator techbench module. This module will test all the possibility case in calculator module with random input numbers (in1 & in2).

The fourth task is hardware validation the small calculator machine. The clock for this module is a debounce button. The inputs in, in2, op are DIP switches. The current state(CS) and the output result(out) are the seven-segment LED.

*Table 4: List of module for task 4*

Module	Function
<b>calculator_FPGA</b>	This is the top-level FPGA hardware module that connects all the necessary module for input switches, buttons, and LEDs.
<b>binary2bcd</b>	This module converts the output result (out) from binary to bcd as ones and tenths value since the maximum result value is 15.
<b>button_debouncer</b>	This module acts as the clock control input
<b>clk_gen</b>	This module produce 5kHz clock signal for the button_debouncer module.
<b>led_mux</b>	This module is taking place in the output of bcd_to_7seg. This module is select the chosen LED to activate.
<b>bcd_to_7seg</b>	This is a decoder module which is convert 4-bit input to 8-bit output .
<b>calculator_constraints</b>	This module set the FPGA pin constraints based on the input/output arrangement specified in the lab instruction.

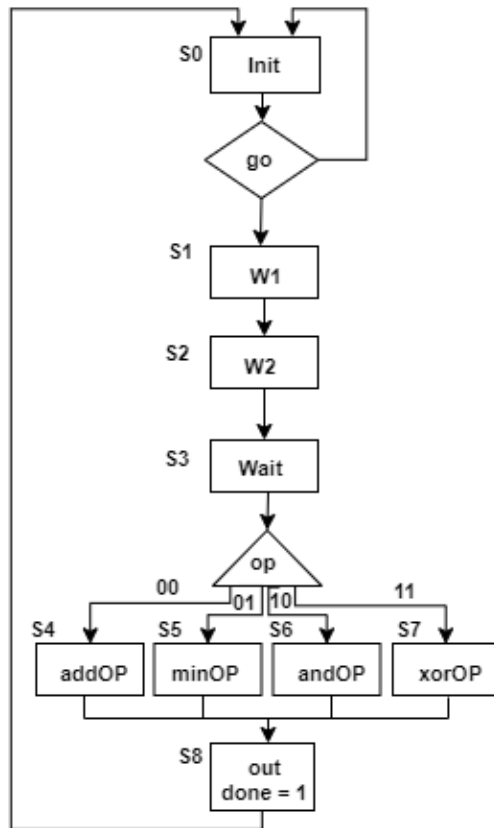


Figure 1: ASM chart describing the Control Unit system's cycle by cycle

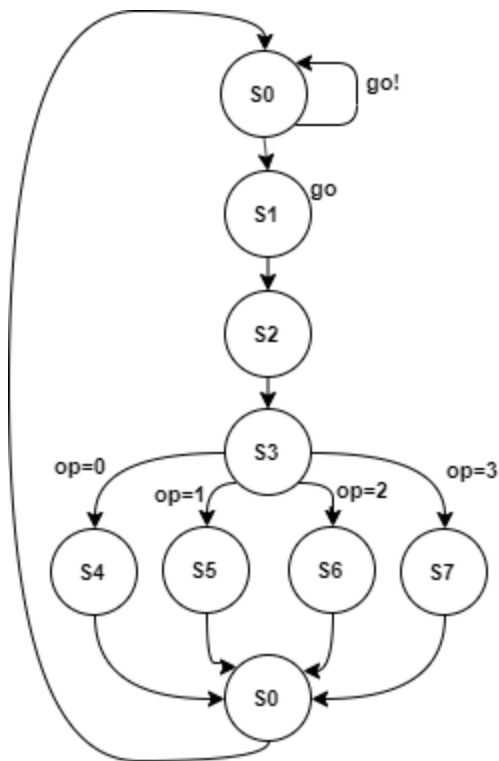


Figure 2: State transition diagram extracted from the ASM chart above

Table 5: Output Logic of the FSM extracted from the ASM chart above

Input		Outputs									
CS	Input name	s1	wa	we	raa	rea	rab	reb	c	s2	done
S0	Init	00	00	0	00	0	00	0	00	0	0
S1	W1	01	01	1	00	0	00	0	00	0	0
S2	W2	10	10	1	00	0	00	0	00	0	0
S3	Wait	00	00	0	00	0	00	0	00	0	0
S4	addOP	11	11	1	01	1	10	1	00	0	0
S5	minOP	11	11	1	01	1	10	1	01	0	0
S6	andOP	11	11	1	01	1	10	1	10	0	0
S7	xorOP	11	11	1	01	1	10	1	11	0	0
S8	out	00	00	0	11	1	11	1	10	1	1

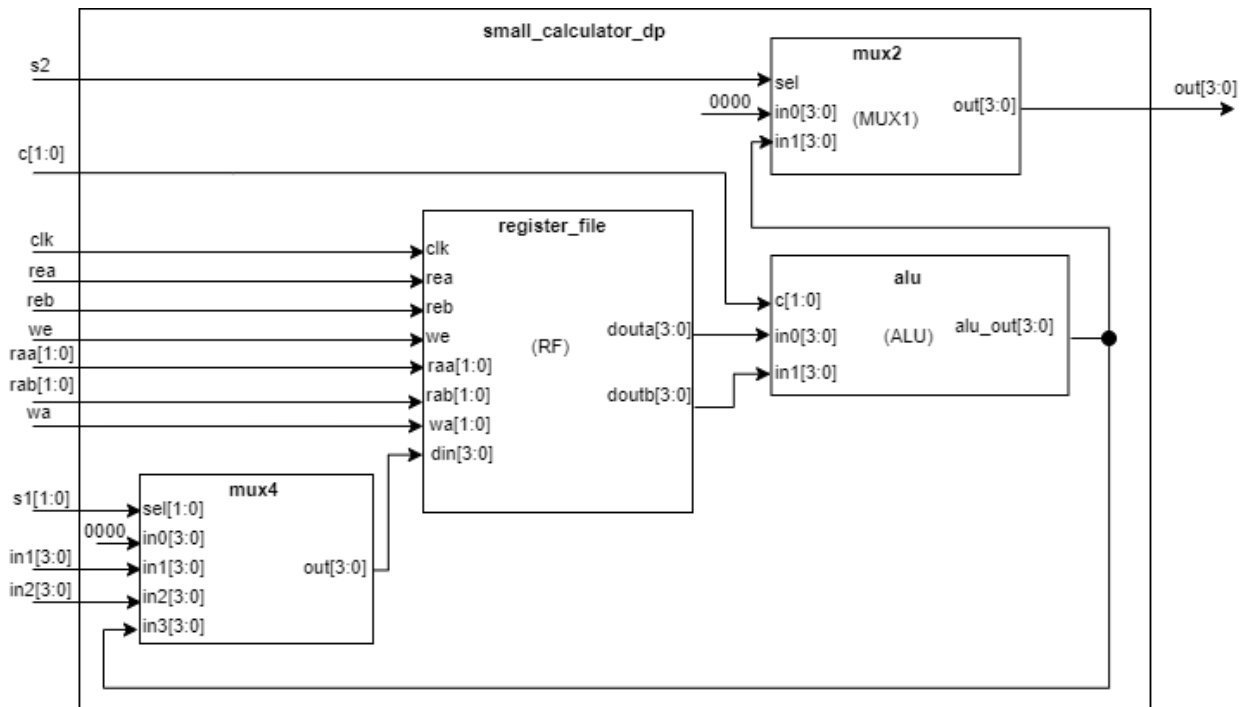


Figure 3: Block diagram for Task 1

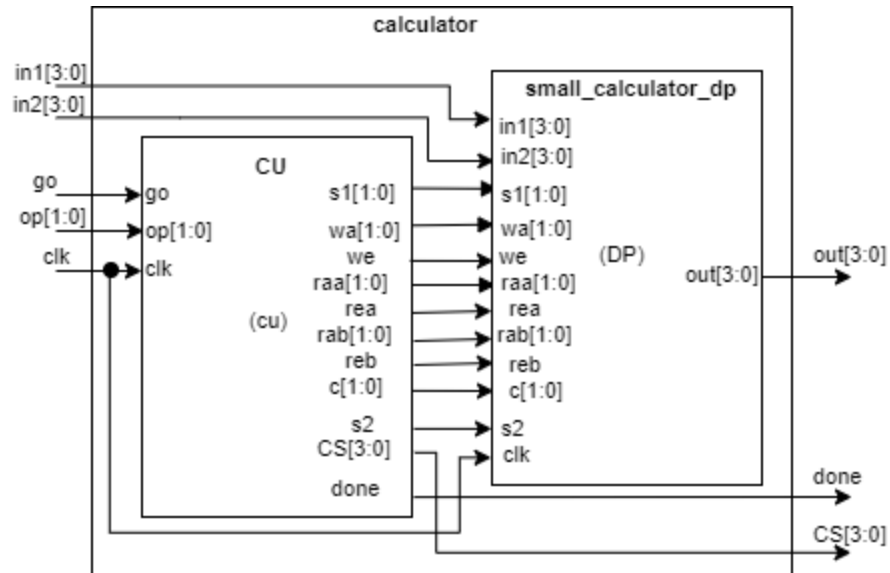


Figure 4:Block diagram for Task 2

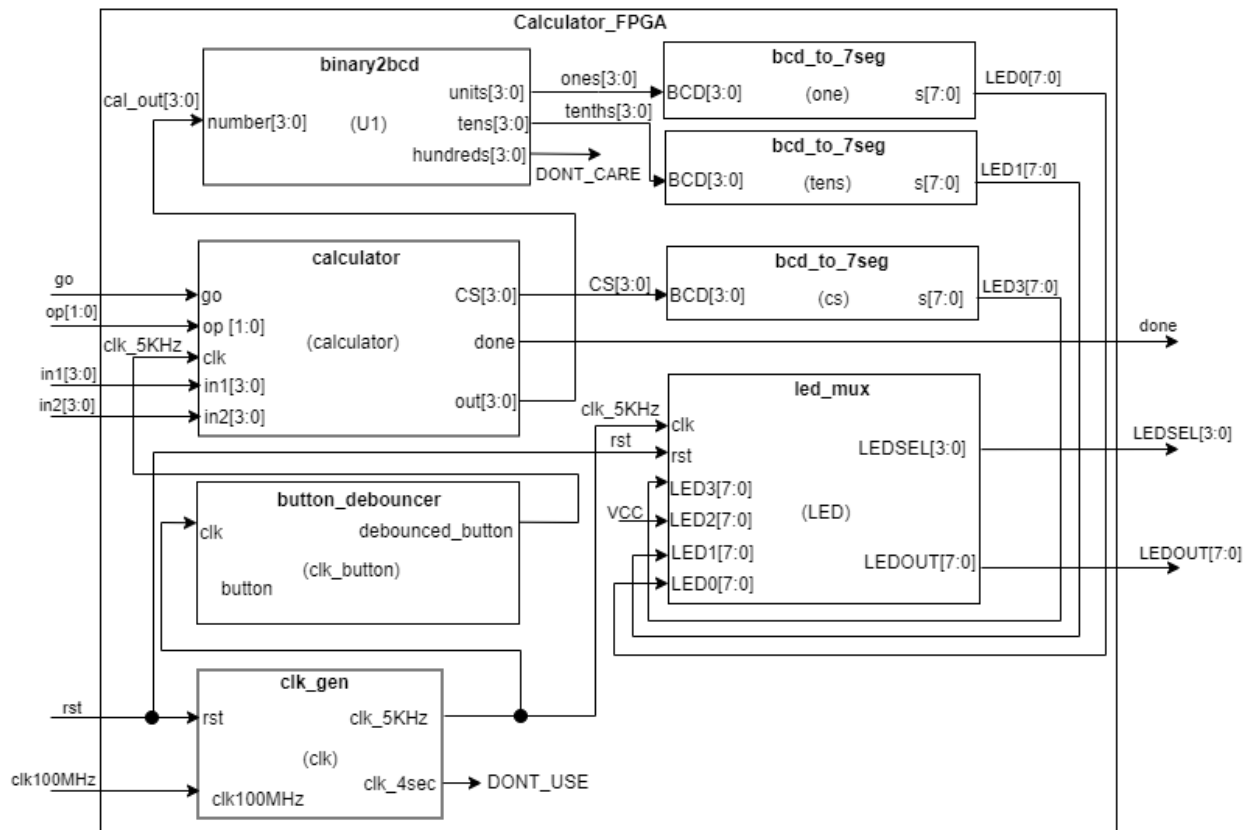


Figure 5:Block diagram for Task 2

## Simulation Result

### Task 1

 


Figure 6: Simulation waveforms produced from Task 1

The testbench for this task would randomly generate 4 combinations of inputs in1 and in2. For each of the input combination, In the first clock cycle, the testbench first store the in1 to the register by setting s1\_tb=01, we\_tb=1, wa\_tb = 01. Then, setting s1=10, wa\_tb = 10 to store in2 data to the register for the next clock cycle. The register module then read out both data inputs by setting raa\_tb=01, rea\_tb=10, rea\_tb=1, and reb\_tb=1. To get the result, the two read inputs then go through the alu. Based on the input operation given by op\_tb, the alu produces the result. In this case, our testbench went through all possible operations from addition(op\_tb =00), subtraction(op\_tb =01), and(op\_tb =10), xor(op\_tb =11). Every time the result received by an operation, it is stored in the register by setting s1\_tb=11, wa\_tb=11 in a clock cycle. Lastly, we output the result by reading out the same address rea\_tb =11, rea\_tb =11, set the alu operation to and(10), and s2=1 in another clock cycle. For instance, the first input was 4(in1\_tb), the second input was 1(in1\_tb). The first two clock cycles were to write them to the register. In the for loop of incrementing operation, the output became 5(4+1), 4-1(3), 0(4&1), 5(4^0) which was as expected. For this reason, the simulation verification was successful.



## Task 2


 


Figure 7: Simulation waveforms produced from Task 2

The testbench for this task would go through all possible operation (op\_tb from 00 to 11) and have go\_tb input signal that always turn high (1) to make the system always go to the next state without interruption from one operation to another. In each of the operation, the testbench would clock 6 times to go from state 0 to state 8. According to *Figure 7*, the output for each state was then compared to the *Output Logic table* observed in *Table 2* above. Since the simulated outputs matched the expected outputs in *Table 2*, the functional verification process for this task was successful.

### Task 3

 

*Figure 8:*Simulation waveforms produced from Task 3

Similar to the above tasks, this testbench go through four random combinations of inputs (in1\_tb&in2\_tb), and all possible input operations(op\_tb) for each input combination (in1\_tb&in2\_tb). Each of the operation also clocked 6 times to go from s0 to s8 state. Since this is a self-checking testbench, it included an expected output (out\_expected) to compare with the actual output (out\_tb). A variable called errors would increment by 1 if the expected output is not equal to the simulated output. According to *Figure 8*, the expected value (out\_expected) matched the actual value(out\_tb), and the errors count was 0. Therefore, the simulated verification process was successful.

### **FPGA Validation**

For the FPGA validation process, the rightmost 4 switches are 4-bit input in1, the leftmost 4 switches are 4bit in2. The middle 2 switches are 2-bit input op(purple). The center button is the clock(yellow), the left button is reset input(green), and the right button is go input(red). Since there are only eight states, the current state output signal (CS) only need one seven segment LED which is on the left. The 4-bit output(out) need two seven segment LED on the right. According to Figure 9, in1 was 0111(7), in2 was 0101(5), and selecting subtraction operation (op=01). The device clocked 6 times after go button was pressed. The result at the last state(s8) was correct since 7-5 is 2. We also randomly tested other input cases and the result also as expected. For this reason, the FPGA validation process was successful.

 


Figure 9: inputs and outputs layout for the FPGA validation process of task 4.

## Conclusion

Overall, both the simulation and FPGA validation process for Task 1 and 2 was successfully performed since the result is as expected. This lab experiment helps strengthen our knowledge on building finite state machine by creating ASM chart, Output Logic table, and State Transition Diagram. We also learn that by functionally verify the data path of any device, we could easily come up with the state machine based on the change of input from the data path. One problem that we met during the testbench is that we could not find the exact amount of clock cycle in one operation. By closely observe the state transitioning, we were able to count the total clock between each state and produce the right simulation.

## Appendix

### a. Source Code

#### Task 1

#### small\_calculator\_dp.v

```
module small_calculator_dp (
    input wire      clk,
    input wire [3:0] in1,
    input wire [3:0] in2,
    input wire [1:0] s1,
    input wire [1:0] wa,
    input wire [1:0] raa,
    input wire [1:0] rab,
    input wire [1:0] c,
    input wire      we,
    input wire      rea,
    input wire      reb,
    input wire      s2,
    output wire [3:0] out
);

wire [3:0] muxlout;
wire [3:0] douta;
wire [3:0] doutb;
wire [3:0] aluout;

mux4 #(
    .WIDTH(4)
) MUX1 (
    .sel      (s1),
    .in0      (4'b0),
    .in1      (in1),
    .in2      (in2),
    .in3      (aluout),
    .out      (muxlout)
);

register_file RF (
    .clk      (clk),
    .rea      (rea),
    .reb      (reb),
    .we       (we),
    .raa      (raa),
    .rab      (rab),
    .wa       (wa),
    .din      (muxlout),
    .douta    (douta),
    .doutb    (doutb)
);

alu ALU (
    .c        (c),
```

```

        .in0      (douta),
        .in1      (doutb),
        .alu_out   (aluout)
    );

    mux2 #(
        .WIDTH(4)
    ) MUX2 (
        .sel       (s2),
        .in0       (4'b0),
        .in1       (aluout),
        .out        (out)
    );

endmodule

```

### **mux4.v**

```

module mux4 #(parameter WIDTH = 4) (
    input  wire [1:0]      sel,
    input  wire [WIDTH-1:0] in0,
    input  wire [WIDTH-1:0] in1,
    input  wire [WIDTH-1:0] in2,
    input  wire [WIDTH-1:0] in3,
    output reg [WIDTH-1:0] out
);

always @ (*) begin
    case(sel)
        2'b00: out = in0;
        2'b01: out = in1;
        2'b10: out = in2;
        2'b11: out = in3;
    endcase
end

endmodule

```

### **register\_file.v**

```

module register_file (
    input wire      clk,
    input wire      rea,
    input wire      reb,
    input wire      we,
    input wire [1:0] raa,
    input wire [1:0] rab,
    input wire [1:0] wa,
    input wire [3:0] din,
    output wire [3:0] douta,
    output wire [3:0] doutb
);

reg [3:0] RegFile[3:0];

always @ (posedge clk) begin
    if(we) begin
        RegFile[wa] <= din;
    end
    else begin
        RegFile[wa] <= RegFile[wa]; //else hold the value
    end
end

assign douta = (rea == 1'b1) ? RegFile[raa] : 4'b0; // when a is enable
assign doutb = (reb == 1'b1) ? RegFile[rab] : 4'b0; //when b is enable

endmodule

```

## alu.v

```

module alu (
    input wire [1:0] c,
    input wire [3:0] in0,
    input wire [3:0] in1,
    output reg  [3:0] alu_out
);

always @ (in0, in1, c) begin
    case(c)
        2'b00: alu_out = in0 + in1;
        2'b01: alu_out = in0 - in1;
        2'b10: alu_out = in0 & in1;
        2'b11: alu_out = in0 ^ in1;
    endcase
end

endmodule

```

## mux2.v

```

module mux2 #(WIDTH = 4) (
    input wire          sel,
    input wire [WIDTH-1:0] in0,
    input wire [WIDTH-1:0] in1,
    output wire [WIDTH-1:0] out
);

    assign out = (sel == 1'b1) ? in1 : in0;

endmodule

```

### small\_calculator\_dp\_tb.v

```

module small_calculator_dp_tb;

    reg      clk_tb;
    reg [3:0] in1_tb;
    reg [3:0] in2_tb;
    reg [1:0] s1_tb;
    reg [1:0] wa_tb;
    reg [1:0] raa_tb;
    reg [1:0] rab_tb;
    reg [1:0] c_tb;
    reg      we_tb;
    reg      rea_tb;
    reg      reb_tb;
    reg      s2_tb;
    wire [3:0] out_tb;

    small_calculator_dp DUT(.clk(clk_tb),
                            .in1(in1_tb),
                            .in2(in2_tb),
                            .s1(s1_tb),
                            .wa(wa_tb),
                            .raa(raa_tb),
                            .rab(rab_tb),
                            .c(c_tb),
                            .we(we_tb),
                            .rea(rea_tb),
                            .reb(reb_tb),
                            .s2(s2_tb),
                            .out(out_tb));

    task ticktock;
    begin
        #5 clk_tb = ~clk_tb;
        #5 clk_tb = ~clk_tb;
    end
endtask

integer i,k;

initial begin
    //initialization

```

```

clk_tb = 0;
s1_tb = 0;
s2_tb = 0;
we_tb = 0;
rea_tb = 0;
reb_tb = 0;
ticktock();
ticktock();

//go through all possible inputs
for(i=0;i<4;i=i+1)
begin
    in1_tb = $random;
    in2_tb = $random;
    we_tb = 1;
    rea_tb = 1;
    reb_tb = 1;//enable all read and write
    s2_tb = 0;// let not output anything first
    //write in1
    s1_tb = 2'b01;
    wa_tb = 2'b01;//write to the address
    ticktock();
    //write in2
    s1_tb = 2'b10;
    wa_tb = 2'b10;//write to the second address
    ticktock();

    for(k = 0; k<4; k = k+1)
    begin
        s2_tb = 1;
        //read number to ALU
        raa_tb = 2'b01;
        rab_tb = 2'b10;
        c_tb = k;// use +/~/&/^
        //go back to Mux1 and write the result to the third location
        s1_tb = 2'b11;//select the result
        wa_tb = 2'b11;//write the result to register3
        ticktock();
        //read the result at the same location
        raa_tb = 2'b11;
        rab_tb = 2'b11;
        c_tb = 2'b10;// use & to output the right number
        ticktock();
    end

    //end
end
end
endmodule

```

## Task 2



## cu.v

```
module CU(input go,
          input clk,
          input [1:0] op,
          output reg [3:0] CS,
          output reg done,
          output reg [1:0] s1, wa, c, raa, rab,
          output reg we, rea, reb, s2
);

parameter Init = 4'b0000, // since the CS is 4 bit
          W1 = 4'b0001,
          W2 = 4'b0010,
          Wait = 4'b0011,
          addOP = 4'b0100,
          minOP = 4'b0101,
          andOP = 4'b0110,
          xorOP = 4'b0111,
          out = 4'b1000;

reg [3:0] NS; //the next state

always@(go,CS,op)
begin
    case(CS)
        Init:
            begin
                if(!go) NS = Init;
                else NS = W1;
            end

        W1:
            begin
                NS = W2;
            end

        W2:
            begin
                NS = Wait;
            end

        Wait:
            begin
                if(op == 2'b00) NS = addOP;
                else if(op == 2'b01) NS = minOP;
                else if(op == 2'b10) NS = andOP;
                else NS = xorOP;
            end

        // transition for each operation
        addOP:
            begin
```

```

        NS = out;
    end

    minOP:
    begin
        NS = out;
    end

    andOP:
    begin
        NS = out;
    end

    xorOP:
    begin
        NS = out;
    end

    //output state
    out:
    begin
        NS = Init;
    end

    default:
    begin
        NS = Init;
    end
endcase
end

//sequential
always@(posedge clk)
    CS <= NS;

always@(CS)
begin
    case(CS)
    Init:
    begin
        s1 = 2'b00;
        s2 = 0;
        we = 0;
        rea = 0;
        reb = 0;
        wa = 2'b00;
        raa = 2'b00;
        rab = 2'b00;
        c = 2'b00;
        done = 0;
    end

    W1:
    begin
        s1 = 2'b01;
        s2 = 0;

```

```
we = 1;
rea = 0;
reb = 0;
wa = 2'b01;
raa = 2'b00;
rab = 2'b00;
c = 2'b00;
done = 0;
end
```

```
W2:
begin
    s1 = 2'b10;
    s2 = 0;
    we = 1;
    rea = 0;
    reb = 0;
    wa = 2'b10;
    raa = 2'b00;
    rab = 2'b00;
    c = 2'b00;
    done = 0;
end
```

```
Wait:
begin
    s1 = 2'b00;
    s2 = 0;
    we = 0;
    rea = 0;
    reb = 0;
    wa = 2'b00;
    raa = 2'b00;
    rab = 2'b00;
    c = 2'b00;
    done = 0;
end
```

```
addOP:
begin
    s1 = 2'b11;
    s2 = 0;
    we = 1;
    rea = 1;
    reb = 1;
    wa = 2'b11;
    raa = 2'b01;
    rab = 2'b10;
    c = 2'b00;
    done = 0;
end
```

```
minOP:
begin
    s1 = 2'b11;
```

```
s2 = 0;
we = 1;
rea = 1;
reb = 1;
wa = 2'b11;
raa = 2'b01;
rab = 2'b10;
c = 2'b01;
done = 0;
end
```

```
andOP:
begin
    s1 = 2'b11;
    s2 = 0;
    we = 1;
    rea = 1;
    reb = 1;
    wa = 2'b11;
    raa = 2'b01;
    rab = 2'b10;
    c = 2'b10;
    done = 0;
end
```

```
xorOP:
begin
    s1 = 2'b11;
    s2 = 0;
    we = 1;
    rea = 1;
    reb = 1;
    wa = 2'b11;
    raa = 2'b01;
    rab = 2'b10;
    c = 2'b11;
    done = 0;
end
```

```
out:
begin
    s1 = 2'b00;
    s2 = 1;
    we = 0;
    rea = 1;
    reb = 1;
    wa = 2'b00;
    raa = 2'b11;
    rab = 2'b11;
    c = 2'b10;
    done = 1;
end
```

```
default:
begin
    s1 = 2'b00;
```

```

        s2 = 0;
        we = 0;
        rea = 0;
        reb = 0;
        wa = 2'b00;
        raa = 2'b00;
        rab = 2'b00;
        c = 2'b00;
        done = 0;
    end

    endcase
end

endmodule

```

## cu\_tb.v

```

module CU_tb;
    reg clk_tb;
    reg go_tb;
    reg [1:0] op_tb;
    wire [3:0] cs_tb;
    wire done_tb;
    wire [1:0] s1_tb;
    wire [1:0] wa_tb;
    wire [1:0] raa_tb;
    wire [1:0] rab_tb;
    wire [1:0] c_tb;
    wire      we_tb;
    wire      rea_tb;
    wire      reb_tb;
    wire      s2_tb;

    CU DUT(.clk(clk_tb),
        .op(op_tb),
        .done(done_tb),
        .go(go_tb),
        .CS(cs_tb),
        .s1(s1_tb),
        .wa(wa_tb),
        .raa(raa_tb),
        .rab(rab_tb),
        .c(c_tb),
        .we(we_tb),
        .rea(rea_tb),
        .reb(reb_tb),
        .s2(s2_tb));

    task ticktock;
    begin
        #5 clk_tb = ~clk_tb;
    end
endmodule

```

```

        #5 clk_tb = ~clk_tb;
    end
endtask

integer i;

initial begin
    go_tb = 0;
    clk_tb = 0;
    op_tb = 2'b00;

    for(i=0; i< 4; i = i+1)
    begin
        op_tb =i;
        go_tb = 1;
        //Init
        ticktock();
        //W1:
        ticktock();
        //W2:
        ticktock();
        //Wait:
        ticktock();
        //op:
        ticktock();
        //out:
        ticktock();
        //Init
        ticktock();

    end
end
endmodule

```

### Task3:

#### calculator.v

```

module calculator(input go,
                  input [1:0] op,
                  input clk,
                  input [3:0] in1,in2,
                  output [3:0] CS,
                  output done,
                  output [3:0] out
);

    wire [1:0] s1, wa, c, raa, rab;
    wire we, rea, reb, s2;

    CU cu(.go(go),
          .op(op),

```

```

        .clk(clk),
        .done(done),
        .CS(CS),
        .s1(s1),
        .wa(wa),
        .c(c),
        .raa(raa),
        .rab(rab),
        .we(we),
        .rea(rea),
        .reb(reb),
        .s2(s2));
    small_calculator_dp DP(.clk(clk),
                           .in1(in1),
                           .in2(in2),
                           .s1(s1),
                           .wa(wa),
                           .raa(raa),
                           .rab(rab),
                           .c(c),
                           .we(we),
                           .rea(rea),
                           .reb(reb),
                           .s2(s2),
                           .out(out));

endmodule

```

### calculator\_tb.v

Work in progress

### Task4:

### calculator\_FPGA.v

```

module calculator_FPGA(input wire go,
    input wire [1:0] op,
    input wire clk100mHz,
    input wire rst,
    input wire [3:0] in1,in2,
    input wire CLK_db,
    output wire done,

```

```

        output wire [3:0] LEDSEL,
        output wire [7:0] LEDOUT
    );

    wire [3:0] CS;
    wire [3:0] cal_out;
    wire DONT_USE;
    wire DONT_CARE, dont_use, dont_care;
    wire clk_5KHz;
    wire debounced_clk;
    wire debounced_rst_button;
    wire [3:0] ones, tenths, CS_bcd;
    wire [7:0] LED3, LED1, LED0;

    supply1 [7:0] vcc;

    clk_gen      clk(.clk100MHz(clk100mHz),
                    .rst(rst),
                    .clk_4sec(DONT_USE),
                    .clk_5KHz(clk_5KHz));

    button_debouncer  clk_button(.clk(clk_5KHz),
                                .button(CLK_db),
                                .debounced_button(debounced_clk));

    calculatorFPGA calculator (.go(go),
                              .op(op),
                              .clk(debounced_clk),
                              .in1(in1),
                              .in2(in2),
                              .CS(CS),
                              .done(done),
                              .out(cal_out));

    binary2bcd U1      (.number(cal_out),
                      .units(ones),
                      .tens(tenths),
                      .hundreds(DONT_CARE));

    bcd_to_7seg      cs (.BCD(CS),
                      .s(LED3));
    bcd_to_7seg      tens(.BCD(tenths),
                      .s(LED1));
    bcd_to_7seg      one(.BCD(ones),
                      .s(LED0));

    led_mux          LED(.clk(clk_5KHz),
                      .rst(rst),
                      .LED3(LED3),
                      .LED2(vcc),
                      .LED1(LED1),
                      .LED0(LED0),
                      .LEDSEL(LEDSEL),
                      .LEDOUT(LEDOUT));

endmodule

```



## clk\_gen.v

```
module clk_gen (
    input wire clk100MHz,
    input wire rst,
    output reg clk_4sec,
    output reg clk_5KHz
);

integer count1, count2;

always @ (posedge clk100MHz) begin
    if (rst) begin
        count1 = 0;
        count2 = 0;
        clk_5KHz = 0;
        clk_4sec = 0;
    end
    else begin
        if (count1 == 200000000) begin
            clk_4sec = ~clk_4sec;
            count1 = 0;
        end

        if (count2 == 10000) begin
            clk_5KHz = ~clk_5KHz;
            count2 = 0;
        end

        count1 = count1 + 1;
        count2 = count2 + 1;
    end
end

endmodule
```

## button\_debouncer.v

```
module button_debouncer #(parameter depth = 16) (
    input wire clk,                /* 5 KHz clock */
    input wire button,             /* Input button from constraints */
    output reg debounced_button
);

localparam history_max = (2**depth)-1;

/* History of sampled input button */
reg [depth-1:0] history;
```

```

always @ (posedge clk) begin
    /* Move history back one sample and insert new sample */
    history <= { button, history[depth-1:1] };

    /* Assert debounced button if it has been in a consistent state
throughout history */
    debounced_button <= (history == history_max) ? 1'b1 : 1'b0;
end

endmodule

```

## binary2bcd.v

```

module binary2bcd(number, hundreds, tens, units);
    // I/O Signal Definitions
    input  [3:0] number;
    output reg [3:0] hundreds;
    output reg [3:0] tens;
    output reg [3:0] units;

    // Internal variable for storing bits
    reg [19:0] shift;
    integer i;

    always @(number)
    begin
        // Clear previous number and store new number in shift register
        shift[19:8] = 0;
        shift[7:0] = number;

        // Loop eight times
        for (i=0; i<8; i=i+1) begin
            if (shift[11:8] >= 5)
                shift[11:8] = shift[11:8] + 3;

            if (shift[15:12] >= 5)
                shift[15:12] = shift[15:12] + 3;

            if (shift[19:16] >= 5)
                shift[19:16] = shift[19:16] + 3;

            // Shift entire register left once
            shift = shift << 1;
        end

        // Push decimal numbers to output
        hundreds = shift[19:16];
        tens      = shift[15:12];
        units     = shift[11:8];
    end
endmodule

```

```
end

endmodule
```

### bcd\_to\_7seg.v

```
module bcd_to_7seg (
    input wire [3:0] BCD,
    output reg [7:0] s
);
    always @ (BCD) begin
        case (BCD)
            4'd0: s = 8'b10000000;
            4'd1: s = 8'b11111001;
            4'd2: s = 8'b10100100;
            4'd3: s = 8'b10110000;
            4'd4: s = 8'b10011001;
            4'd5: s = 8'b10010010;
            4'd6: s = 8'b10000010;
            4'd7: s = 8'b11111000;
            4'd8: s = 8'b10000000;
            4'd9: s = 8'b10010000;
            default: s = 8'b01111111;
        endcase
    end
endmodule
```

### led\_mux.v

```
module led_mux (
    input wire clk,
    input wire rst,
    input wire [7:0] LED3,
    input wire [7:0] LED2,
    input wire [7:0] LED1,
    input wire [7:0] LED0,
    output wire [3:0] LEDSEL,
    output wire [7:0] LEDOUT
);
    reg [1:0] index;
    reg [11:0] led_ctrl;
    assign {LEDSEL, LEDOUT} = led_ctrl;
    always @ (posedge clk) index <= (rst) ? 2'b0 : (index + 2'd1);
    always @ (index, LED0, LED1, LED2, LED3) begin
        case (index)
            4'd0: led_ctrl <= {4'b1110, LED0};
            4'd1: led_ctrl <= {4'b1101, LED1};
            4'd2: led_ctrl <= {4'b1011, LED2};
            4'd3: led_ctrl <= {4'b0111, LED3};
            default: led_ctrl <= {8'b1111, 8'hFF};
        endcase
    end
endmodule
```

```

endcase
end
endmodule

```

## calculator\_constraints.xdc

```

# Clock signal
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33}
[get_ports {clk100mHz}];
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5}
[get_ports {clk100mHz}];

# input switches
#input1
set_property -dict {PACKAGE_PIN V17 IOSTANDARD LVCMOS33} [get_ports
{in1[0]}];
set_property -dict {PACKAGE_PIN V16 IOSTANDARD LVCMOS33} [get_ports
{in1[1]}];
set_property -dict {PACKAGE_PIN W16 IOSTANDARD LVCMOS33} [get_ports
{in1[2]}];
set_property -dict {PACKAGE_PIN W17 IOSTANDARD LVCMOS33} [get_ports
{in1[3]}];
#input2
set_property -dict {PACKAGE_PIN W2 IOSTANDARD LVCMOS33} [get_ports
{in2[0]}];
set_property -dict {PACKAGE_PIN U1 IOSTANDARD LVCMOS33} [get_ports
{in2[1]}];
set_property -dict {PACKAGE_PIN T1 IOSTANDARD LVCMOS33} [get_ports
{in2[2]}];
set_property -dict {PACKAGE_PIN R2 IOSTANDARD LVCMOS33} [get_ports
{in2[3]}];

#clock button
set_property -dict {PACKAGE_PIN U18 IOSTANDARD LVCMOS33} [get_ports
{CLK_db}];
#go button
set_property -dict {PACKAGE_PIN T17 IOSTANDARD LVCMOS33} [get_ports {go}];
#reset button
set_property -dict {PACKAGE_PIN W19 IOSTANDARD LVCMOS33} [get_ports {rst}];

#op switches
set_property -dict {PACKAGE_PIN V2 IOSTANDARD LVCMOS33} [get_ports
{op[1]}];
set_property -dict {PACKAGE_PIN W13 IOSTANDARD LVCMOS33} [get_ports
{op[0]}];

set_property -dict {PACKAGE_PIN L1 IOSTANDARD LVCMOS33} [get_ports {done}];
# output LED

#LED selection
set_property -dict {PACKAGE_PIN U2 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[0]}]; # AN0

```

```

set_property -dict {PACKAGE_PIN U4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[1]}}; # AN1
set_property -dict {PACKAGE_PIN V4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[2]}}; # AN2
set_property -dict {PACKAGE_PIN W4 IOSTANDARD LVCMOS33} [get_ports
{LEDSEL[3]}}; # AN3

#LED output
set_property -dict {PACKAGE_PIN W7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[0]}}; # CA
set_property -dict {PACKAGE_PIN W6 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[1]}}; # CB
set_property -dict {PACKAGE_PIN U8 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[2]}}; # CC
set_property -dict {PACKAGE_PIN V8 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[3]}}; # CD
set_property -dict {PACKAGE_PIN U5 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[4]}}; # CE
set_property -dict {PACKAGE_PIN V5 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[5]}}; # CF
set_property -dict {PACKAGE_PIN U7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[6]}}; # CG
set_property -dict {PACKAGE_PIN V7 IOSTANDARD LVCMOS33} [get_ports
{LEDOUT[7]}}; # DP

```